Performing Arithmetic&Logic Operations on Quantum Computer

Ali Hakim Taşkiran Department of Electrical&Electronics Engineering

What is Logic?

"The science of thinking about or explaining the reason for something using formal methods."[1]

Logic enables us to relate and link statements.

Statement

"Something that you say or write that gives information or an opinion."[1]

- "Ankara is capital of Turkey" (True)
- "Books are printed on paper" (True)
- "Inconsistent behaviour is consistent" (False)

Role of Statements in Logic

Reality may be unreal and it may be real.

Logic Gate


Logic Gate Symbols OR NOR AND NAND **XOR XNOR** Buffer NOT

NOT

"used to give the following word or phrase a negative meaning"[1]

I did **not** buy **apple**

A	A'
1	0
0	1

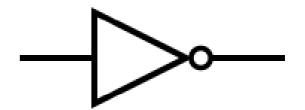


AND

"Used to connect words or parts of sentences"[1]

I bought apple and banana from market

*Both of them

Α	В	A&B
1	1	1
1	0	0
0	1	0
0	0	0

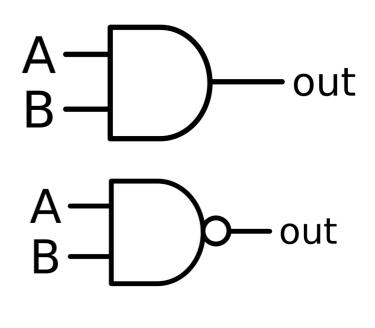


OR

"Used to introduce another possibility"[1]

I bought apple or banana from market

Α	В	A B	A
1	1	1	В
1	0	1	
0	1	1	A
0	0	0	В

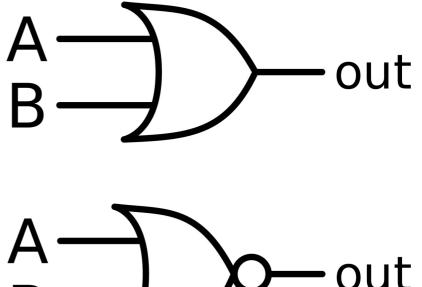


XOR(Either)

"One or the other of two; it does not matter which"[1]

I bought **either apple or banana** from market

*Not both and not none of them


Α	В	A⊕B
1	1	0
1	0	1
0	1	1
0	0	0

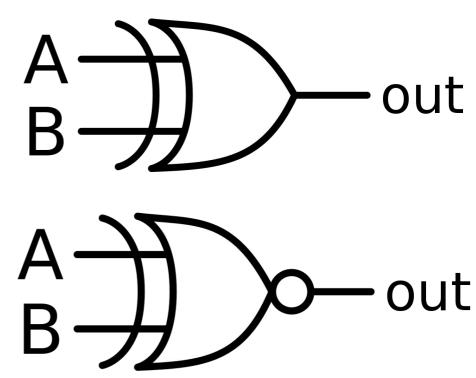



What Is Arithmetic?


"The type of mathematics that deals with the adding, multiplying, etc. of numbers."[1]


Expressing Numbers in Binary

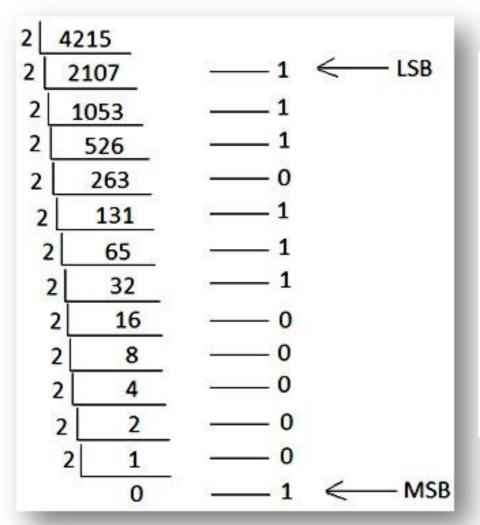


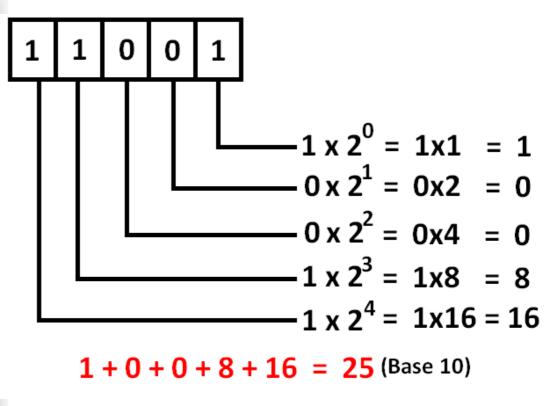

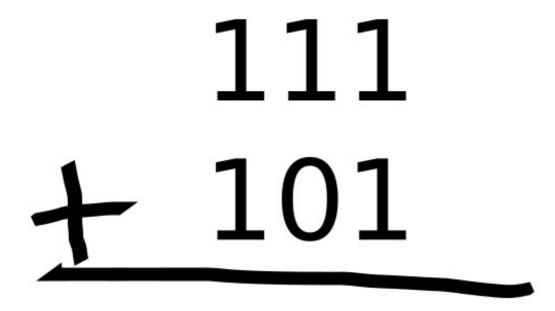

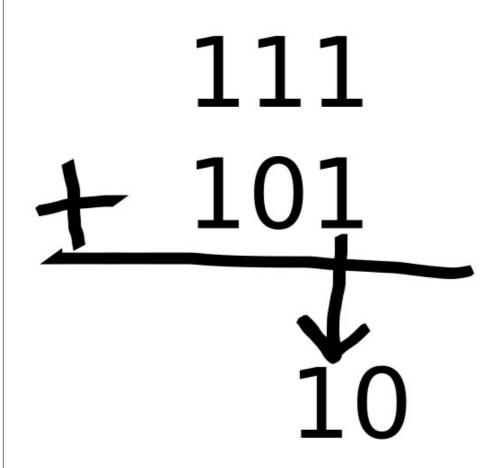


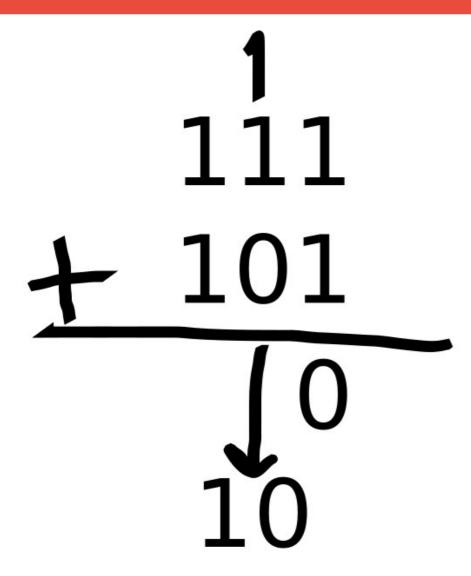

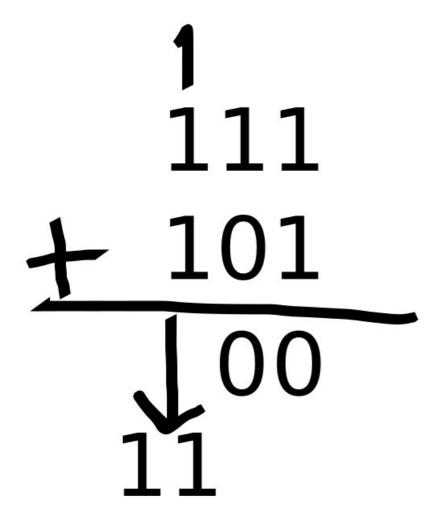

A	В	Carry	Sum
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	0

Half Adder

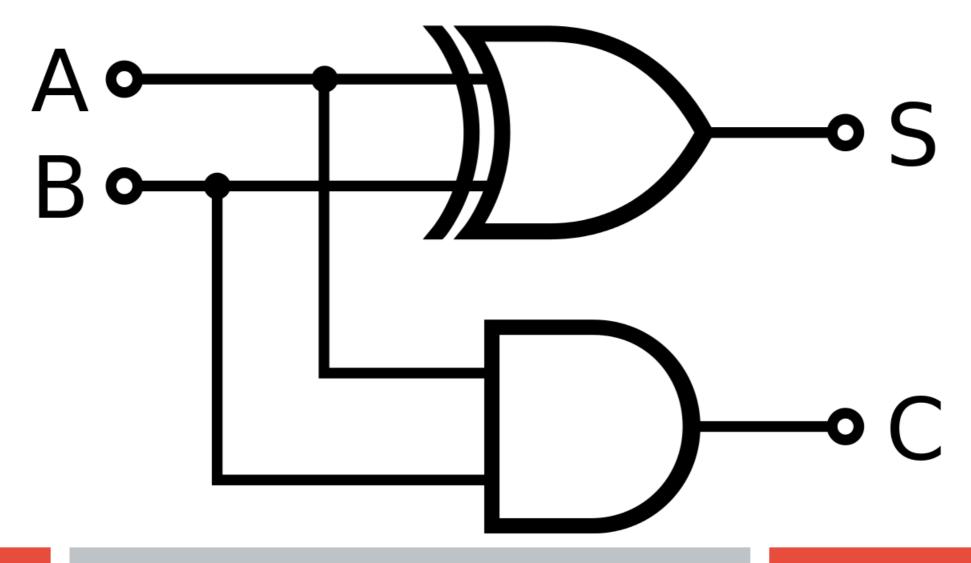

What If We Add Carry?


We will no longer perform A+B+Carry operation with 2 inputs.


We need a new circuit for adding three addend

Full Adder

Α	В	<u>C</u> _{in}	Ç _{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder

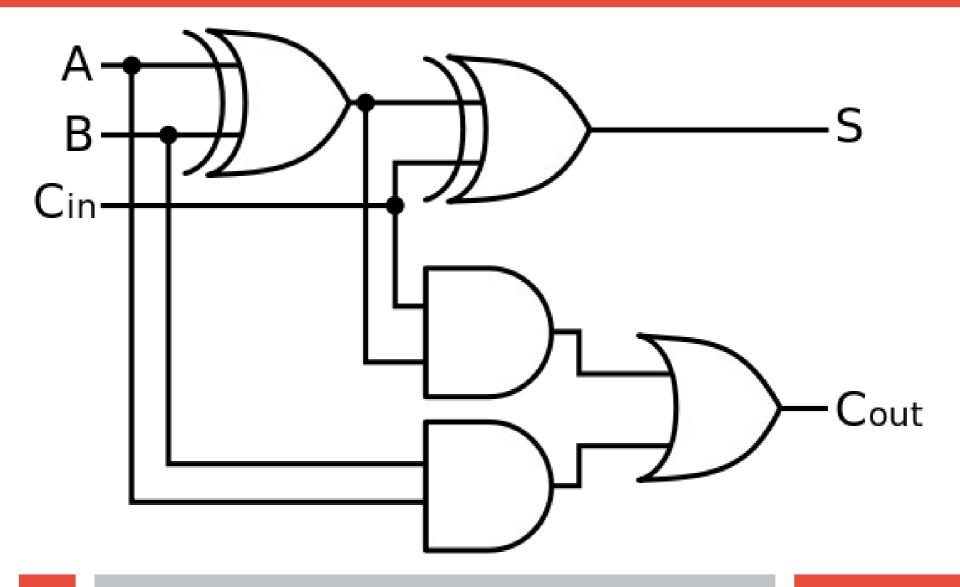


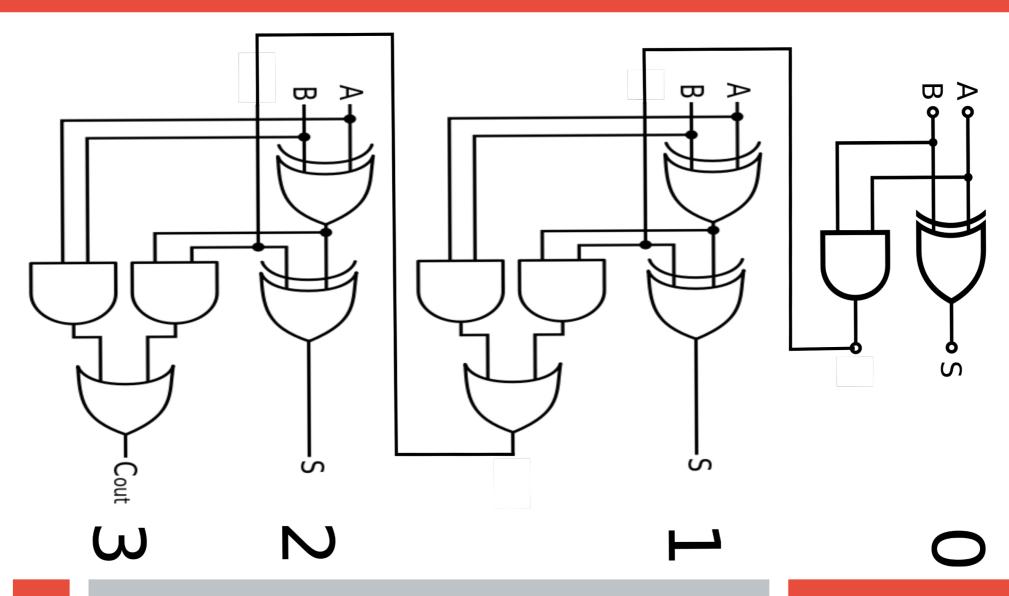


Using Quantum Mechanics

Quantum mechanics accelerates addition insanely.

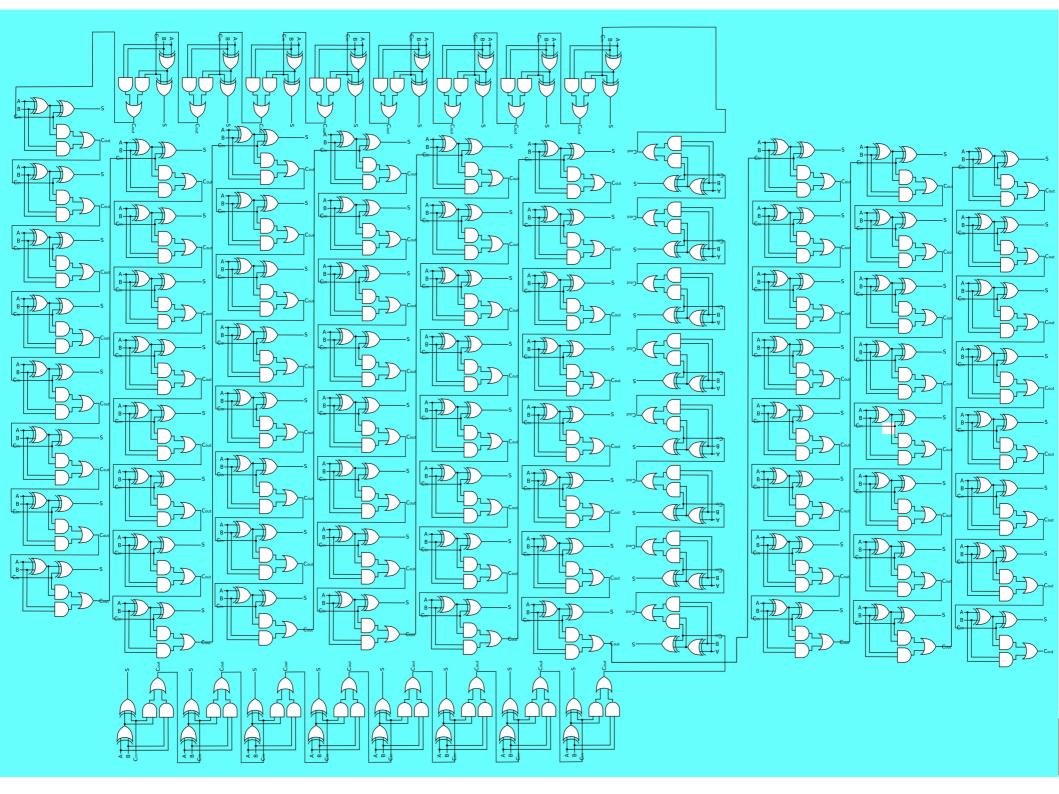We are able to perform 64 summing operations in the same instance if we use previous adder circuit.



Quantum Adder

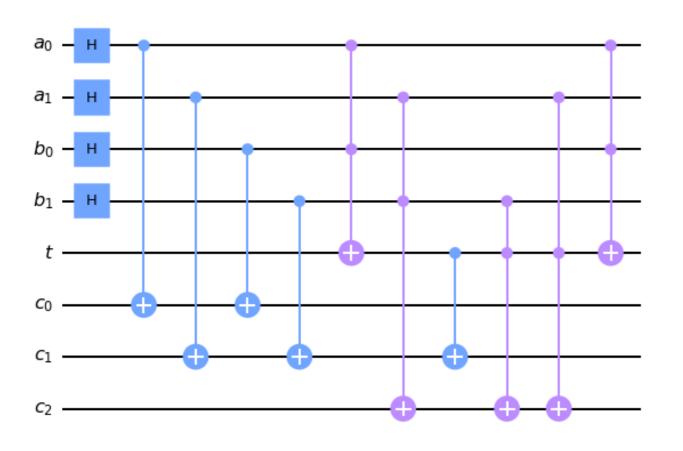

```
0=0+0 00000-0000-0000
0=1+3 00000-0001-0011
0=3+1 00000-0011-0001
1=0+1 00001-0000-0001
1=1+0 00001-0001-0000
2=0+2 00010-0000-0010
2=1+1 00010-0001-0001
2=2+0 00010-0010-0000
3=0+3 00011-0000-0011
3=1+2 00011-0001-0010
3=2+1 00011-0010-0001
3=3+0 00011-0011-0000
4=2+2 00100-0010-0010
5=2+3 00101-0010-0011
5=3+2 00101-0011-0010
6=3+3 00110-0011-0011
16
```

References

[1] OxfordLearningDictionaries, viewed 21 Oct 2021, <

https://www.oxfordlearnersdictionaries.com/ >

Thank you for your time