Performing Arithmetic&Logic Operations on Quantum Computer

Ali Hakim Taşkiran Department of Electrical&Electronics Engineering

What is Logic?

"The science of thinking about or explaining the reason for something using formal methods."[1]

Logic enables us to relate and link statements.

Statement

"Something that you say or write that gives information or an opinion."[1]

- "Ankara is capital of Turkey" (True)
- "Books are printed on paper" (True)
- "Inconsistent behaviour is consistent" (False)

Role of Statements in Logic


Reality may be unreal and it may be real.

NOT

"used to give the following word or phrase a negative meaning"[1]

I did **not** buy **apple**

| A | A' |
|---|----|
| 1 | 0 |
| 0 | 1 |

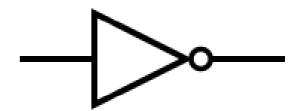


AND

"Used to connect words or parts of sentences"[1]

I bought apple and banana from market

*Both of them

| Α | В | A&B |
|---|---|-----|
| 1 | 1 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 0 | 0 | 0 |

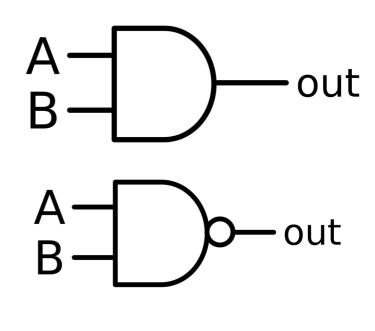


OR

"Used to introduce another possibility"[1]

I bought apple or banana from market

| Α | В | A B | $A \longrightarrow$ |
|---|---|--------|--------------------------|
| 1 | 1 | 1 | $B \longrightarrow \int$ |
| 1 | 0 | 1 | |
| 0 | 1 | 1 | $A \longrightarrow$ |
| 0 | 0 | 0 | B - I |

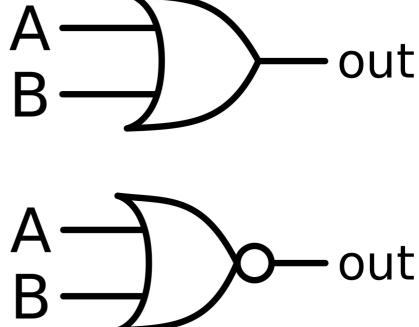


XOR(Either)

"One or the other of two; it does not matter which"[1]

I bought **either apple or banana** from market

*Not both and not none of them


| Α | В | A⊕B |
|---|---|-----|
| 1 | 1 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 0 | 0 | 0 |

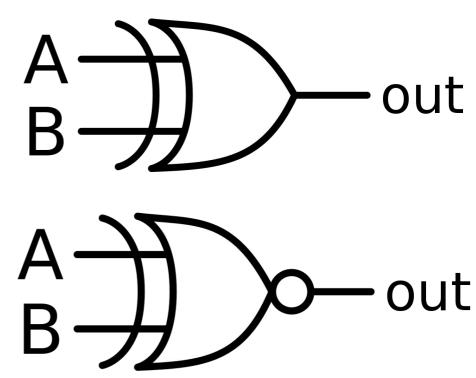



What Is Arithmetic?


"The type of mathematics that deals with the adding, multiplying, etc. of numbers."[1]


Expressing Numbers in Binary

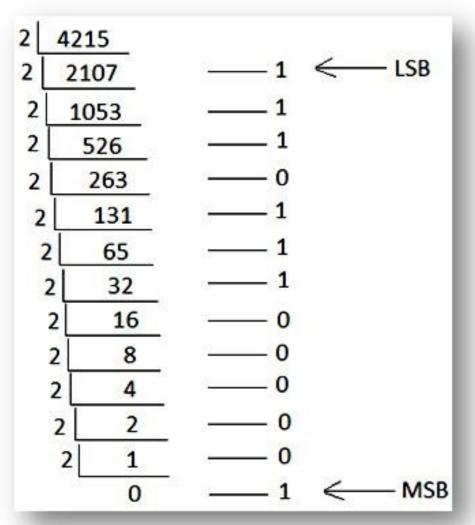


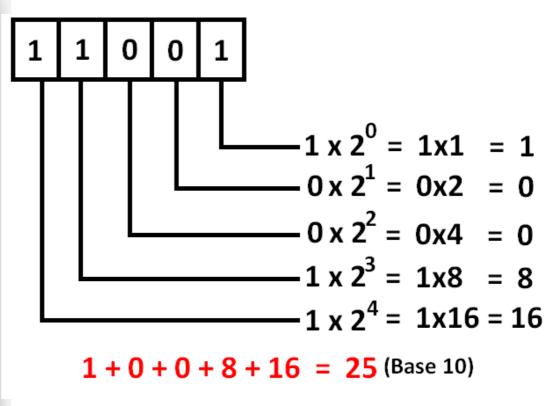


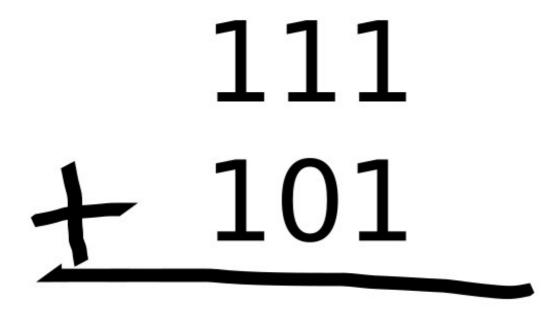

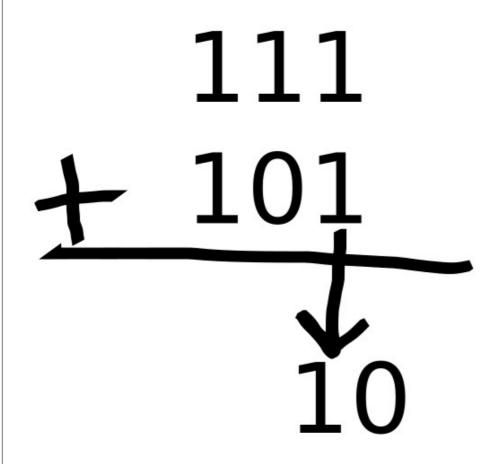

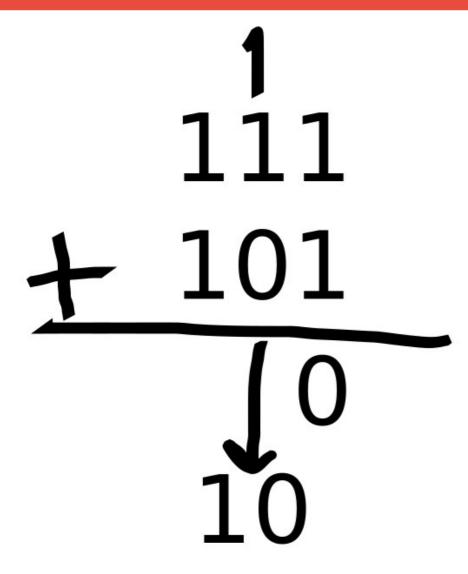


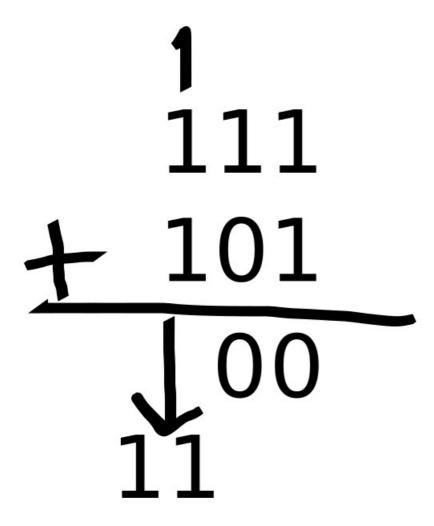

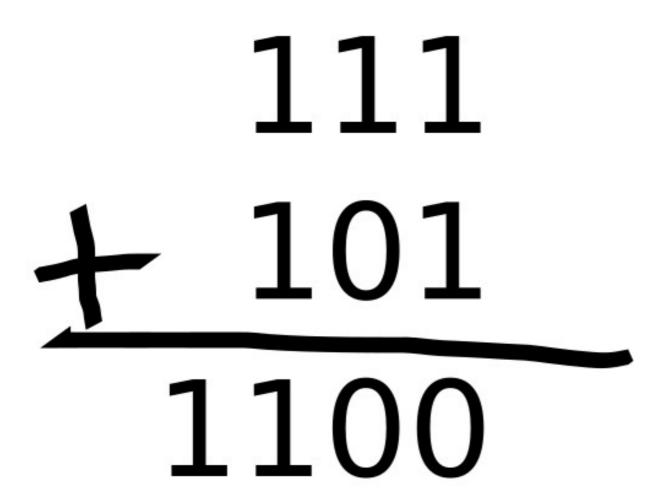

| A | В | Carry | Sum |
|---|---|-------|-----|
| 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 |

Half Adder

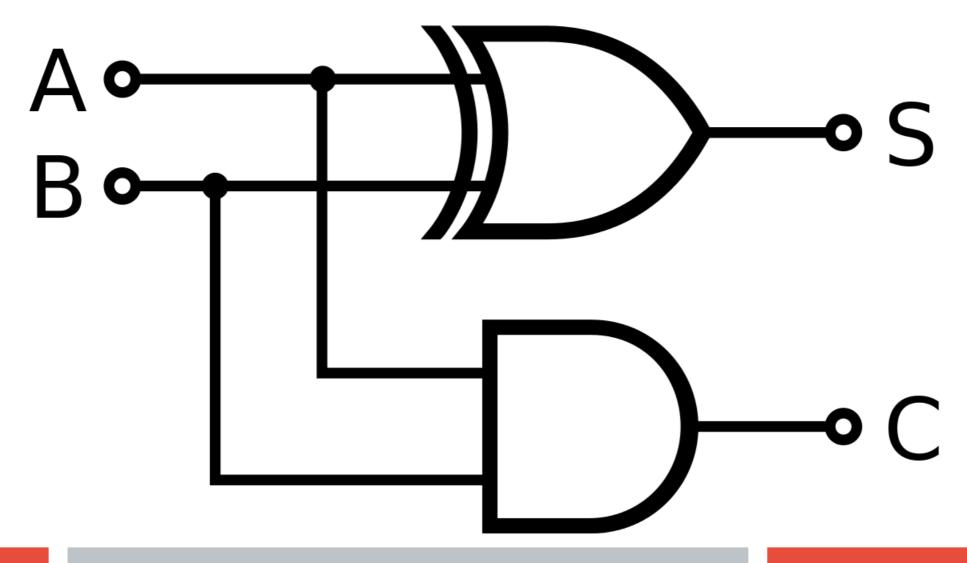

What If We Add Carry?


We will no longer perform A+B+Carry operation with 2 inputs.


We need a new circuit for adding three addend

Full Adder

| Α | В | <u>C</u> _{in} | C _{out} | Sum |
|---|---|------------------------|------------------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder

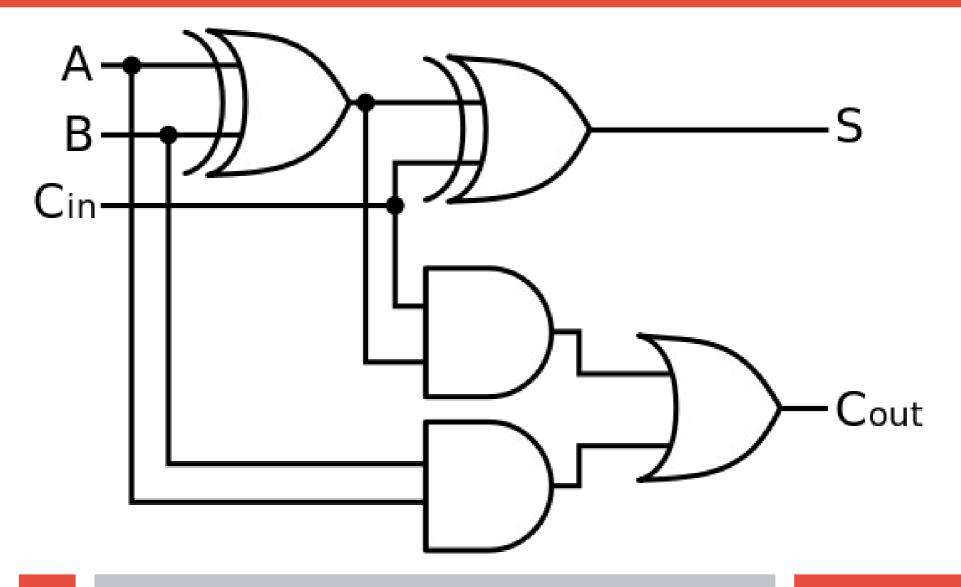


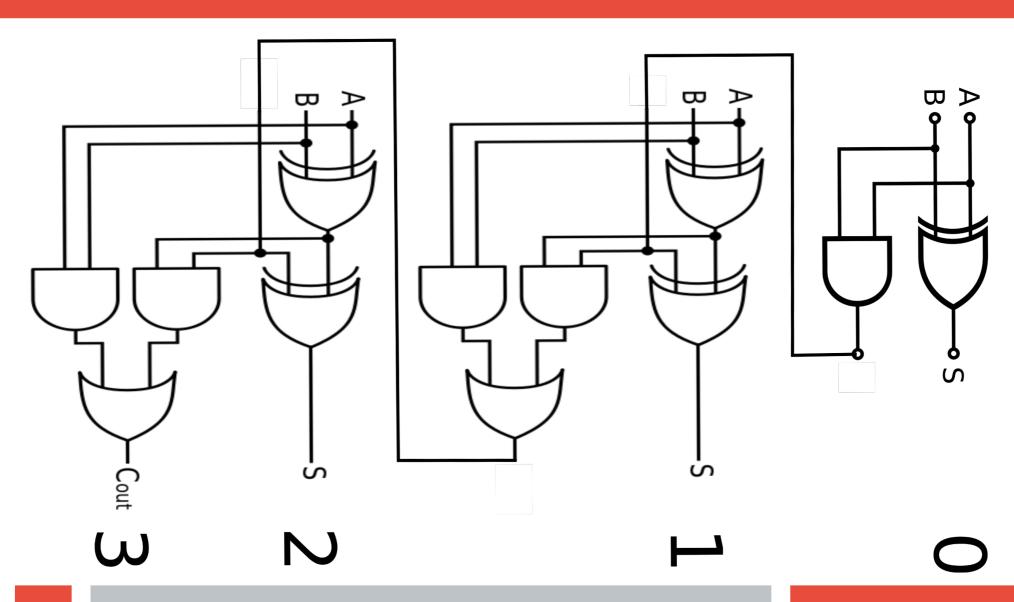


Using Quantum Mechanics

Quantum mechanics accelerates addition insanely.

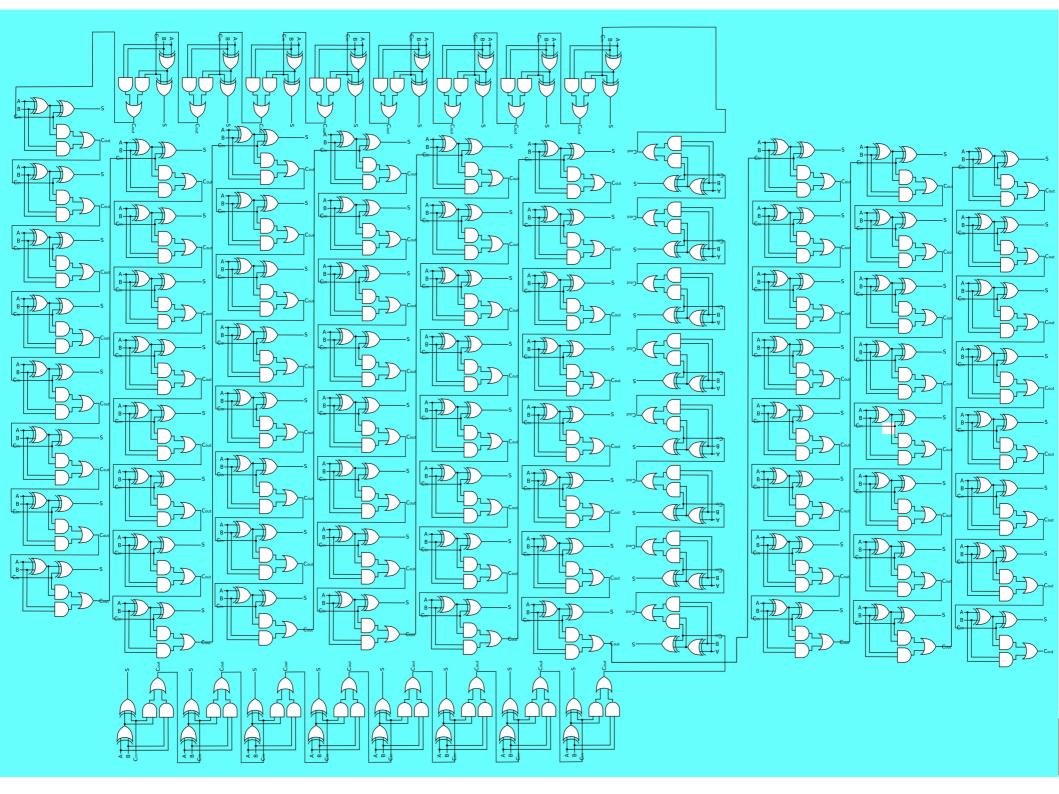We are able to perform 64 summing operations in the same instance if we use previous adder circuit.



Quantum Adder

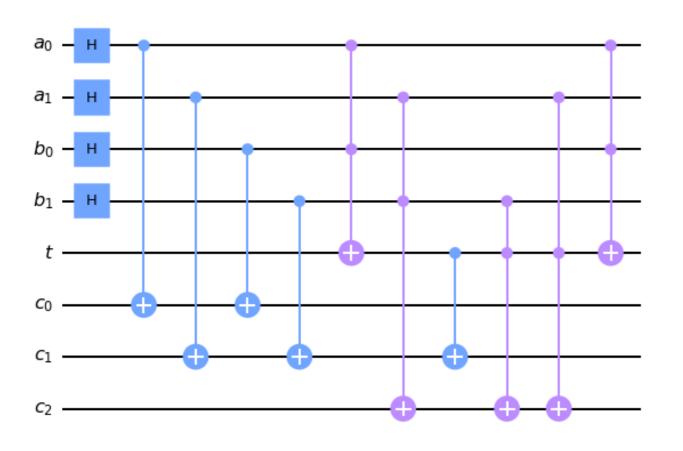

```
0=0+0 00000-0000-0000
0=1+3 00000-0001-0011
0=3+1 00000-0011-0001
1=0+1 00001-0000-0001
1=1+0 00001-0001-0000
2=0+2 00010-0000-0010
2=1+1 00010-0001-0001
2=2+0 00010-0010-0000
3=0+3 00011-0000-0011
3=1+2 00011-0001-0010
3=2+1 00011-0010-0001
3=3+0 00011-0011-0000
4=2+2 00100-0010-0010
5=2+3 00101-0010-0011
5=3+2 00101-0011-0010
6=3+3 00110-0011-0011
16
```

References

[1] OxfordLearningDictionaries, viewed 21 Oct 2021, <

https://www.oxfordlearnersdictionaries.com/ >

Thank you for your time